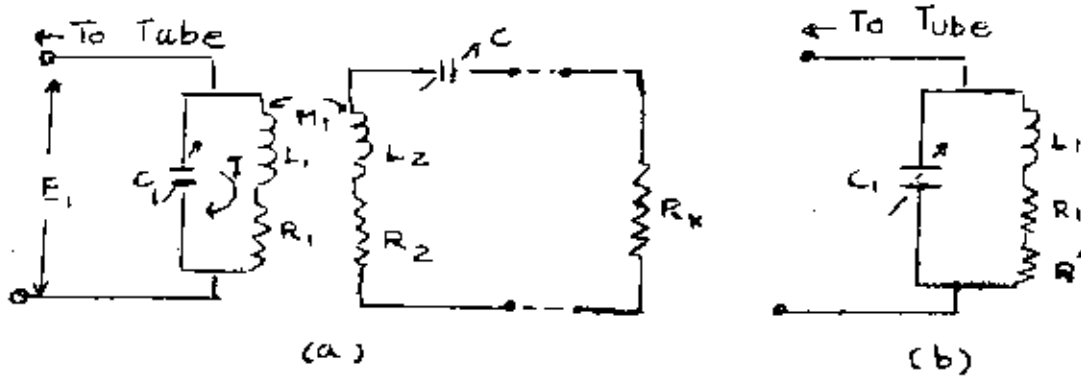


บทที่ 10

THE RESONANCE LOAD CIRCUIT (1)



รูปที่ 1 Resonance Load Circuit ของ Oscillator

R_1 = Resistance ของ Coil L_1

R_2 = Resistance ของ Coil L_2

R_X = Resistance ของ Load

จากรูปที่ 1 (a), C_2 , L_2 , R_2 และ R_X เป็น Load ที่ coupling กับ C_1 , L_1 , R_1 ของ oscillator

ที่ resonance angular frequency (ω_r) impedance ของ L_2 , C_2 , R_2 และ R_X จะเป็น pure resistance และจะ reflect กลับมายัง resonance circuit ของ L_1 , C_1 และ จะได้ reflected resistance คือ

$$R' = \frac{\omega_r^2 M^2}{R_2 + R_X} \dots \dots \dots (1)$$

ดังนั้น Circuit ของรูปที่ 1 (a) จึงเขียนเสียใหม่ตามรูปที่ 1 (b)

(1) Ryder, John D, Engineering Electronics with Industrial Application and Control, pp. 375 - 377

Resistance Load ของ Oscillator จึงประกอบไปด้วย R_1 ซึ่งเป็น resistance ของ Coil L_1 และ R_1

$$R = R_1 + R'$$

$$= R_1 + \frac{(wr)^2 M^2}{R_2 + R_X} \dots \dots \dots (2)$$


เมื่อ $wr = \frac{1}{\sqrt{L_1 C_1}} \dots \dots \dots (3)$

สำหรับ Tuned Plate Oscillator จะ Oscillate ได้เมื่อ

$$\bar{G}_m \geq \frac{M C_1 R}{M M - L_1} \dots \dots \dots (4)$$

เมื่อ $M =$ mutual inductance ระหว่าง grid กับ plate ดังนั้นการคำนวณหา reflected resistance (R_T) ของบทที่ 3 จึงต้องคิด reflected resistance ของ L_{11} และ L_{12} ด้วย

วิธีหาค่า R_T

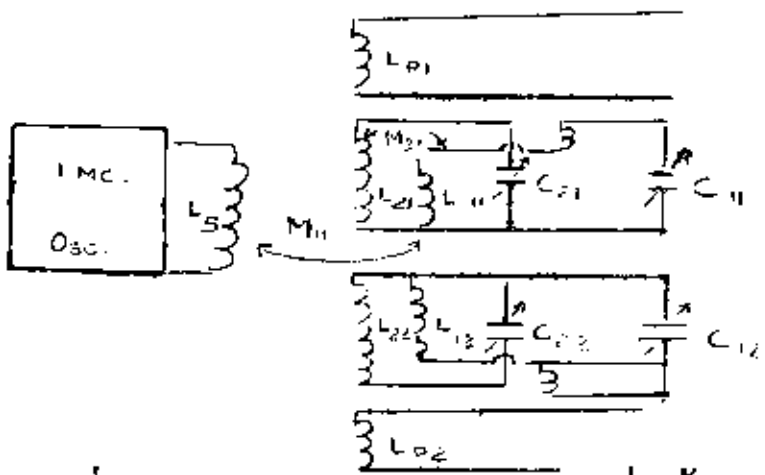

รูปที่ 2 Circuit ของ Electrol เพื่อหา R_T

ถ้าคิดว่า CORE NO.1 และ NO.2 เหมือนกันทั้งค่า R, L และ M ค่าความ reflected resistance ของ circuit เดียว โดยเอาค่าเฉลี่ยของ R, M ของทั้งสอง air core ดังนี้

$$M_{11} = \frac{0.430 + 0.518}{2} = 0.474 \text{ mH.}$$

$$M_{31} = \frac{0.370 + 0.577}{2} = 0.473 \text{ mH.}$$

$$R_{11} = \frac{12.60 + 12.60}{2} = 12.60 \ \Omega$$

$$R_{21} = \frac{8.90 + 6.20}{2} = 7.55 \ \Omega$$

$$R_5 = 5.84 + 6.20 = 12.04 \ \Omega$$


- เมื่อ R_{11} = resistance ของ coil L_{11}
 R_{21} = resistance ของ coil L_{21}
 R_5 = resistance ของ coil L_5 ($L_5 = L_{51} + L_{52}$)

ถ้า Oscillator ให้ resonance frequency = 1 MC.


$$\begin{aligned} \therefore \omega_r &= 2\pi f_r \\ &= 2\pi \times 1 \times 10^6 \\ &= 6.28 \times 10^6 \end{aligned}$$

จากรูปที่ 2 ถ้า reflect R_{21} ของ L_{21}, C_{21} ไปยัง L_{11}, C_{11} ตามรูปที่ 3
 จะได้ R_{11} ต่อ series กับ R_{11} เมื่อ
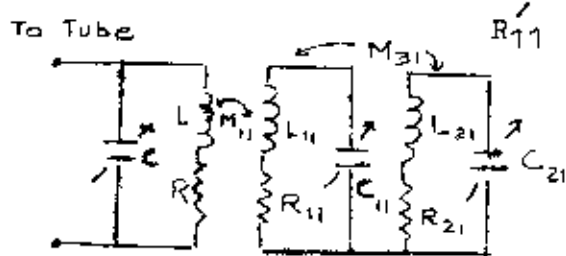
$$R'_{11} = \frac{\omega_r^2 M_{31}^2}{R_{21}}$$



(a)

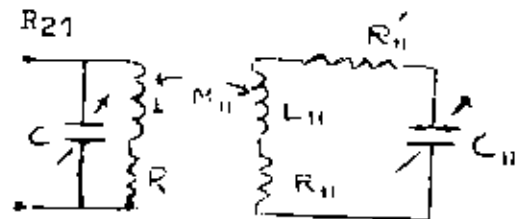

(b)

รูปที่ 3 แสดงการคิด R_T

$$L = L_5 + L_4 = 2 + 0.25 = 2.25 \text{ mH.}$$

$$R = R_5 + R_4 = 13.04 + 2.5 = 15.54 \ \Omega$$

$$\begin{aligned}\therefore R'_{11} &= \frac{[(6.28 \times 10)^6 (0.473) \times 10^{-3}]^2}{8.70} \\ &= \frac{8.80 \times 10^6}{8.70} \\ &= 1.01 \times 10^6 \quad \Omega\end{aligned}$$

ในทางตรงกันข้าม ถ้า reflect R_{11} , R'_{11} ไปใน circuit ของ L, R จะได้ reflected resistance = R' และต้องคูณด้วยสอง เพราะมีสอง coupling-circuit

$$\begin{aligned}\therefore R' &= 2 \times \frac{(W_r M_{11})^2}{R_{11} + R'_{11}} \quad \text{ohms} \\ &= 2 \times \frac{(6.28 \times 10^6 \times 0.474 \times 10^{-3})^2}{12.60 + 1.01 \times 10^6} \quad \text{ohms} \\ &= 2 \times \frac{8.84 \times 10^6}{1.01 \times 10^6} \quad \text{"} \\ &= 2 \times 8.74 \quad \text{"} \\ &= 17.48 \quad \text{"}\end{aligned}$$

∴ Resistance load ของ oscillator (R_T)

$$\begin{aligned}R_T &= R + R' \\ &= 15.54 + 17.48 \\ \underline{R_T} &= \underline{33.02} \quad \text{ohms}\end{aligned}$$

บรรณานุกรม



- (1) Archer, K.R. "Humidity and Moisture Measurement", Far East Engineering and Equipment News, Far East Trade Press Publication, September, 1965.
 - (2) Burton, Malcolm S. Applied Metalurgy for Engineers, McGraw-Hill Book Comp., New York.
 - (3) Chate, George M. Electronics in Industry, 2nd. ed., McGraw-Hill Book Comp., New York, Toronto, London.
 - (4) Gray, Truman S. Applied Electronics, Mordern Asia Edition, 2nd. ed., Charles E. Tuttle Company, Tokyo.
 - (5) Harrison, N.J. RCA Receiving Tube Manual, Technical Series RC - 23, Radio Corporation of America.
 - (6) Heine, Richard W., Rosenthal, Phillip. C. Principle of Metal Casting. McGraw-Hill Book Comp., New York (1955).
 - (7) Henney, Keith. Radio Engineering Handbook, 4th. ed., McGraw-Hill Book Comp., New York, Toronto, London.
 - (8) Markus, John and Zeluff, Vin. Handbook of Industrial Electronics, McGraw-Hill Book Comp., New York.
 - (9) Ryder, John D. Engineering Electronics with Industrial and Application Control, Asian Students' Edition, Kogakusha Company, Ltd., Tokyo.
 - (10) Soisson, Harold E. Electronics Measuring Instruments, McGraw-Hill Book Comp., New York, Toronto, London (1961).
 - (11) Terman, Frederic Emmous. Radio Engineering Handbook, 1st.ed., McGraw-Hill Book Comp., New York, London (1943).
 - (12) Terman, Frederic Emmous. Radio Engineering, 2nd. ed., McGraw-Hill Book Comp., New York, London (1937).
-